

# Analog IC Design

## Lab 05

### Simple vs Low Compliance Cascode Current Mirror

## Part 1: Sizing Chart

$V^*=200$  mV

$V_{DD}=1.8$  V


$I_{ref}=20$   $\mu$ A

$W=10$   $\mu$ M

$L=1$   $\mu$ M

**Plot  $V^*$  and  $V_{ov}$  overlaid vs  $V_{GS}$ . Make sure the y-axis of both curves has the same range, Locate the point at which  $V^*=200$  mV. Find the corresponding  $V_{ovQ}$  and  $V_{GSQ}$ .**


For NMOS

 

$V_{gsq}=610.7$  mV

$V_{ovq}=206.3$  mV

For PMOS

 


$V_{gsq}=606.5$  mV

$V_{ovq}=-195.5$  mV

**Plot  $I_D$ ,  $g_m$ , and  $g_{ds}$  vs  $V_{GS}$ . Find their values at  $V_{GSQ}$ . Let's name these values  $I_{DX}$ ,  $g_{mX}$ , and  $g_{dsX}$ .**

### **Plots for NMOS**

 


$I_{DX}=47.1 \text{ uA}$

$g_{mX}=0.462 \text{ mS}$

$g_{dsX}=3.643 \text{ uS}$

### **Plots for PMOS**

 

$I_{DX}=-11.99 \text{ uA}$

$g_{mX}=0.1081 \text{ mS}$

$g_{dsX}=0.9119 \text{ uS}$

Therefore we can use the cross multiplication to calculate the  $W_n, W_p$  of the mosfets

$$W_N = 10 \mu \cdot 20 \mu / 47.1 \mu = 4.246 \text{ uM}$$

$$W_P = 10 \mu \cdot 10 \mu / 11.99 \mu = 16.68 \mu \text{M}$$

Now we are almost done with the design of the amplifier. Note that  $g_m$  is also proportional to  $W$  as long as  $V_{ov}$  is constant. On the other hand,  $r_o = 1/g_{ds}$  is inversely proportional to  $W$  ( $I_D$ ) as long as  $L$  is constant. Before leaving this part, calculate  $g_{mQ}$  and  $g_{dsQ}$  using ratio and proportion (cross-multiplication).

For NMOS:


Gmx=0.2954 mS                      gdsq=1.5468 uS                      ro=646.488 Kohm

For PMOS:


Gmq=196.99 uS                      gdsq=1.521 uS                      ro=657.44 kohm
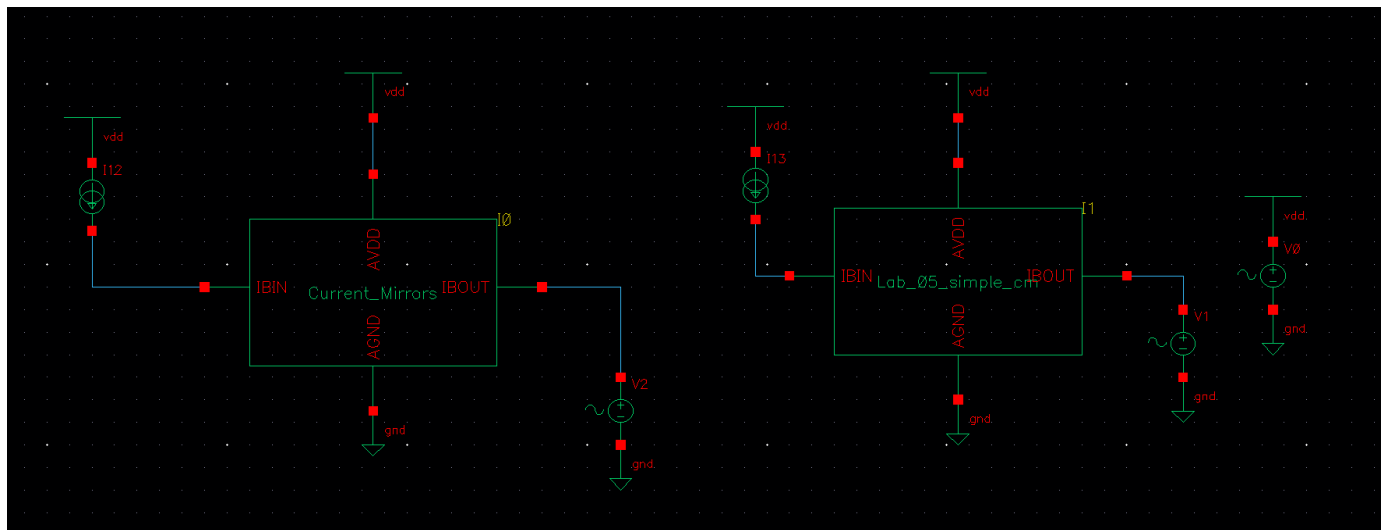
## PART 2: Current Mirror

Schematic of the two CMs with DC node voltages clearly annotated at  $V_{OUT} = V_{DD}/2$  (double click the symbol to go to lower level of hierarchy and show the schematic).



## Current mirror wide-swing:

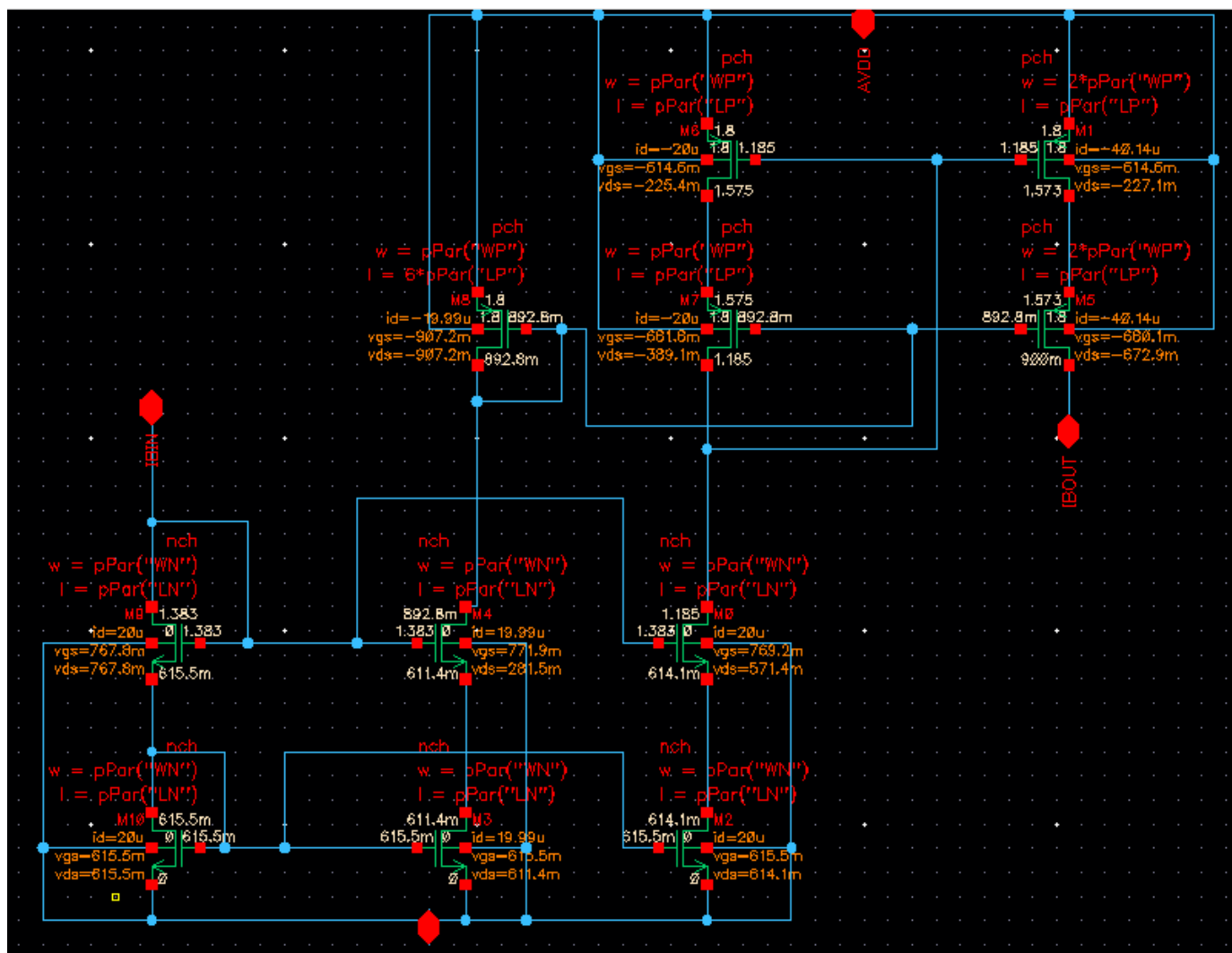

The circuit schematic shows a 3-stage CMOS amplifier. The input stage (M0, M1) is a differential pair with a tail current source (M2). The second stage (M3, M4) is a differential pair with a tail current source (M5). The output stage (M6, M7) is a differential pair with a tail current source (M8). The circuit is biased with VDD and GND. Simulation results show the input and output waveforms.

	A																		B
1																			
2																			
3	Name	/I0/M0	/I0/M1	/I0/M10	/I0/M2	/I0/M3	/I0/M4	/I0/M5	/I0/M6	/I0/M7	/I0/M8	/I0/M9	/I1/M0	/I1/M4	/I1/M5	/I1/M6	/I1/M7	/I1/M8	
4	cd	-1.973i	-25.56f	-1.974f	-1.974f	-1.974f	-2.158f	-21.99f	-12.81f	-11.21f	-11.55f	-1.963f	-1.963f	-11f	-21.94f	-1.974f	-1.972f	-1.974f	
5	cs	-28.73f	-226.4f	-29.24f	-29.24f	-29.24f	-28.78f	-225.4f	-113.2f	-112.8f	-644.2f	-28.71f	-28.71f	-112.9f	-225.6f	-29.24f	-28.73f	-29.24f	
6	cds	1.828u	14.2u	1.694u	1.695u	1.697u	3.942u	3.154u	7.239u	1.993u	221.9u	1.699u	1.699u	1.639u	3.13u	1.694u	1.823u	1.695u	
7	gm	202.5u	384.7u	198.1u	198.1u	198.1u	199.6u	393.4u	191.6u	194.4u	70.92u	203u	203u	198.5u	405.2u	198.1u	202.5u	198.1u	
8	amoverid	10.13	9.584	9.907	9.907	9.908	9.981	9.901	9.579	9.722	3.547	10.15	10.15	9.925	9.873	9.907	10.13	9.907	
9	ld	20u	-40.14u	20u	20u	19.99u	19.99u	-40.14u	-20u	-20u	-19.99u	20u	20u	-20u	-41.04u	20u	20u	20u	
10	region	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	
11	type	0	1	0	0	0	0	1	1	1	0	2	2	1	0	0	0	0	
12	yds	571.4m	-227.1m	615.5m	614.1m	611.4m	281.5m	-672.9m	-225.4m	-389.1m	-907.2m	767.8m	767.8m	-609.8m	-609.8m	-900m	615.5m	576.1m	
13	ydsat	165.4m	-171.1m	158.6m	158.6m	158.6m	166.6m	-172.4m	-170.6m	-173.6m	-409.8m	165m	165m	-167m	-167.5m	158.6m	165.4m	158.6m	
14	yqs	769.2m	-614.6m	615.5m	615.5m	615.5m	771.9m	-680.1m	-614.6m	-681.8m	-907.2m	767.8m	767.8m	-609.8m	-609.8m	615.5m	769.2m	615.5m	
15	yth	576.5m	-411.1m	405.9m	405.9m	406m	577.5m	-483.3m	-411.1m	-482.6m	-380.9m	575.7m	575.7m	-411.1m	-411.1m	405.9m	576.5m	405.9m	
16																			
17																			
18	Region 0 is cutoff.																		
19	Region 1 is linear.																		
20	Region 2 is saturation.																		
21	Region 3 is subthreshold.																		
22	Region 4 is breakdown.																		
23																			
24	Type 0 is nMOS.																		
25	Type 1 is pMOS.																		
26																			
27																			

### Check that all transistors have $V_{GS}$ , $g_m$ and $g_{ds}$ as designed in Part 1


All mosfets which are either bulks connected to the ground (the mosfets at the bottom layer of the schematic) or their bulks connected to the VDD (the PMOS at the top layer of the schematic) they are almost as the designed ones in part 1

While the other mosfets which have their body terminal floating suffer from the body effect which will increase their  $V_{th}$  and then decrease their  $V_{ov}$  so to sustain the same overdrive voltage their  $V_{gs}$  increases.
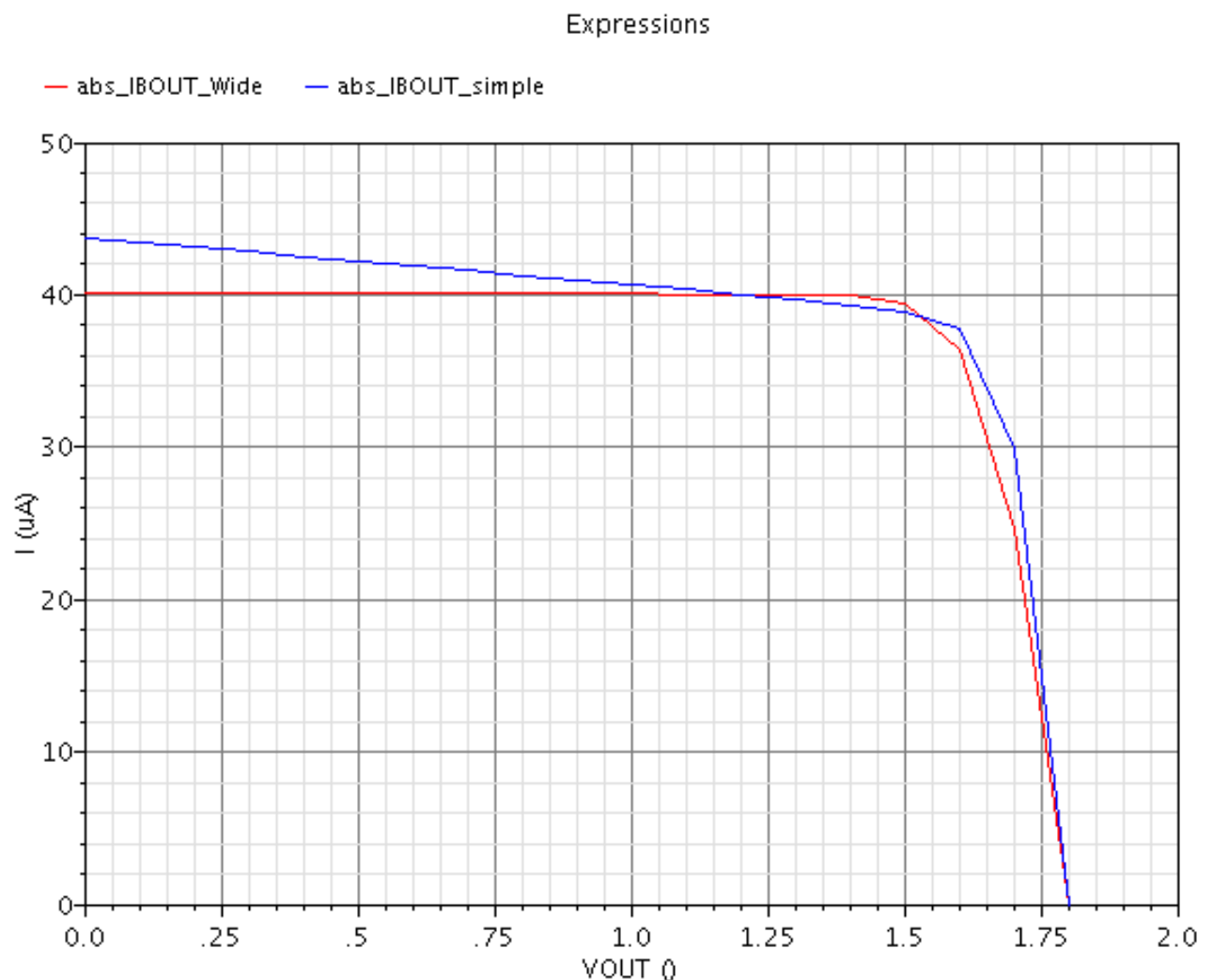
### Are all transistors operating in saturation?

Yes, all transistors are in region 2 (saturation)

Perform DC sweep (not parametric sweep) using  $V_{OUT} = 0:10m:V_{DD}$ . Report  $I_{BOUT}$  vs  $V_{OUT}$  for the two CMs overlaid in the same plot.



### Comment on the difference between the two circuits.


The wide-swing CM gives more accurate result which is almost 40 uA while the simple CM gives a little bit of an error in its output current.

But both current mirrors fail after some point where some mosfets will get out of saturation

**IBOUT of the simple CM is exactly equal to IBIN\*2 at a specific value of VOUT. Why?**

Because at this specific point,  $V_{ds}$  of the two mirror mosfets are the same so there won't be any mismatch error the the mirroring will be more accurate as  $V_{gs}$  is the same and  $V_{ds}$  is the same.

 
**Percent of error in IBOUT vs VOUT (ideal IBOUT should be IBIN\*2) for the two CMs in the current mirror operating region (VOUT = 0 to VDD -  $V_{*}$ ) overlaid in the same plot.**



**Comment on the difference between the two circuits.**

The wide-swing current mirror has better efficiency than the simple current mirror so the error in the wide-swing is less than the simple current mirror and also the simple current mirror has lower Rout.

 **Rout vs VOUT (take the inverse of the derivative of IBOUT plot) for the two CMs in the current mirror operating region (VOUT = 0 to VDD -  $V_{*}$ ) overlaid in the same plot. Use log scale on the y-axis. Add a cursor at VOUT = VDD/2.**



The red curve is the wide-swing CM and the blue is the simple CM

#### Comment on the difference between the two circuits.

From the graph, Rout of the wide-swing CM is much higher than that of the simple CM

Rout\_simple is in the order of  $r_{o5}$

Rout\_WS is in the order of  $g_{m5} r_{o5}^2$

These results above are calculated exactly in the analytical solution so I used it here

#### Does Rout change with VOUT? Why?

yes, because Vout is the Vds of the output mosfet so as vout changes vds changes so the transistor either go deeper into saturation or towards the edge of saturation which will change the value of  $r_o$ .

#### Analytically calculate Rout of both circuits at VOUT = VDD/2. Compare with simulation results in a table.

$$R_{out_{simple}} = R_{LFD_{M5}} = r_{o5}(1 + g_{m5}R_{s5})$$

$$R_{s5} = 0$$

$$R_{out_{simple}} = r_{o5} = \frac{1}{g_{ds5}} = 319.488k\Omega$$

//Rout\_simple is in the order of  $r_{o5}$

$$R_{out_{WS}} = R_{LFD_{M5}} = r_{o5}(1 + g_{m5}R_{s5})$$

$$R_{s5} = R_{LFD_{M1}} = r_{o1}$$

$$R_{out_{WS}} = R_{LFD_{M5}} = r_{o5}(1 + g_{m5}r_{o1}) = r_{o5} * r_{o1} * g_{m5} = 8.7833M\Omega$$



//Rout\_WS is in the order of  $gm(ro)^2$

	Analytically	Simulated
Wide-swing	$8.7833M\Omega$	$11.82 M\Omega$
Simple	$319.488k\Omega$	$319.7k\Omega$